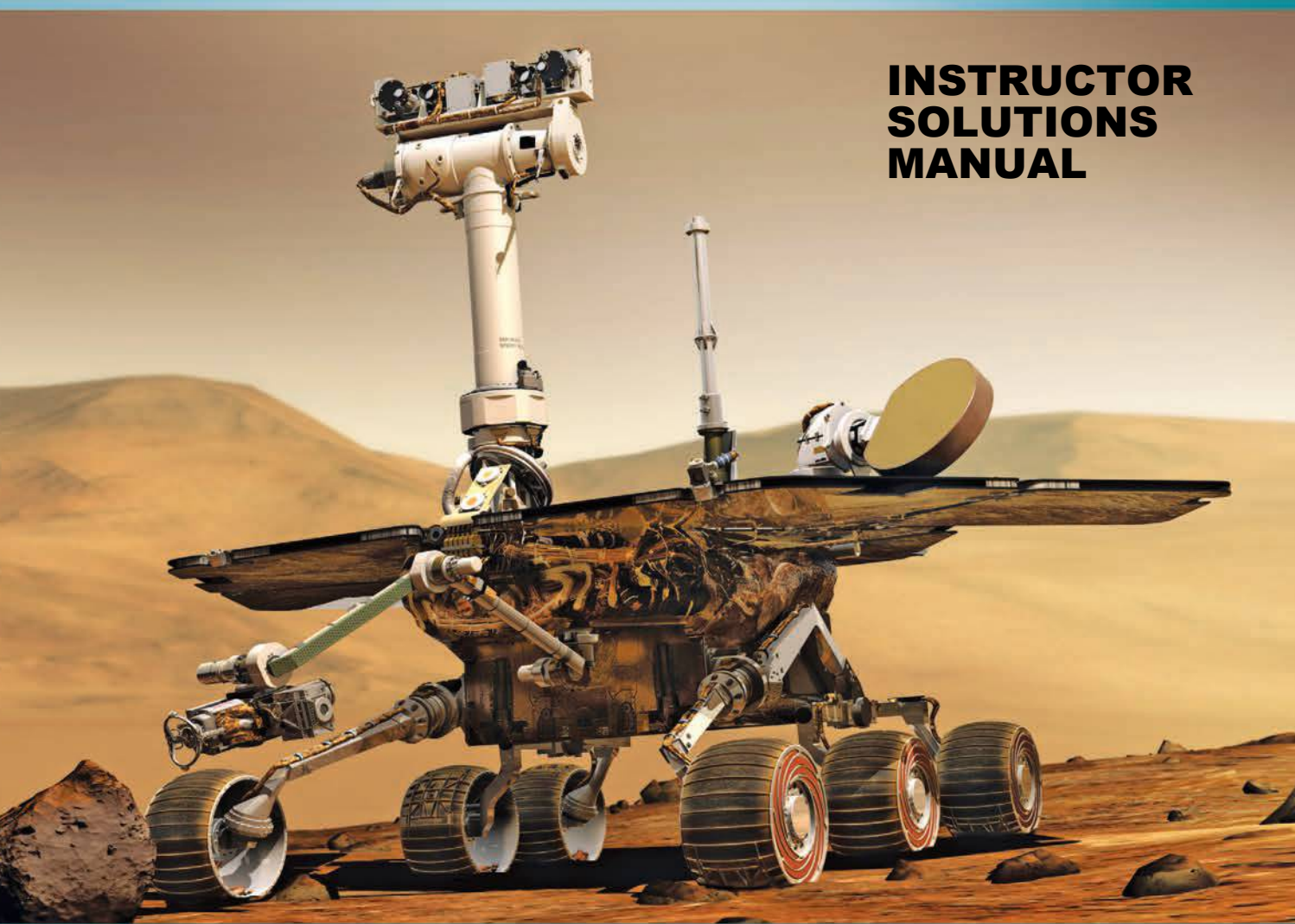


FIFTH EDITION

Fundamentals of Electric Circuits

**INSTRUCTOR
SOLUTIONS
MANUAL**



Charles K. Alexander | Matthew N. O. Sadiku

Chapter 1, Solution 1

(a) $q = 6.482 \times 10^{17} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-103.84 \text{ mC}}$

(b) $q = 1.24 \times 10^{18} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-198.65 \text{ mC}}$

(c) $q = 2.46 \times 10^{19} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-3.941 \text{ C}}$

(d) $q = 1.628 \times 10^{20} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-26.08 \text{ C}}$

Chapter 2, Solution 1. Design a problem, complete with a solution, to help students to better understand Ohm's Law. Use at least two resistors and one voltage source. Hint, you could use both resistors at once or one at a time, it is up to you. Be creative.

Although there is no correct way to work this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

The voltage across a 5-k Ω resistor is 16 V. Find the current through the resistor.

Solution

$$v = iR \qquad i = v/R = (16/5) \text{ mA} = \mathbf{3.2 \text{ mA}}$$

Chapter 3, Solution 1

Using Fig. 3.50, design a problem to help other students to better understand nodal analysis.

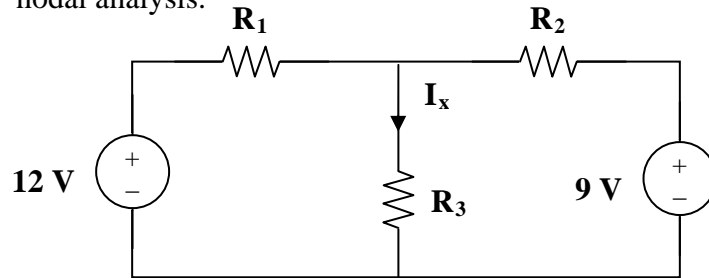


Figure 3.50
For Prob. 3.1 and Prob. 3.39.

Solution

Given $R_1 = 4\text{ k}\Omega$, $R_2 = 2\text{ k}\Omega$, and $R_3 = 2\text{ k}\Omega$, determine the value of I_x using nodal analysis.


Let the node voltage in the top middle of the circuit be designated as V_x .

$$[(V_x - 12)/4k] + [(V_x - 0)/2k] + [(V_x - 9)/2k] = 0 \text{ or (multiply this by 4 k)}$$

$$(1 + 2 + 2)V_x = 12 + 18 = 30 \text{ or } V_x = 30/5 = 6 \text{ volts and}$$

$$I_x = 6/(2k) = \mathbf{3\text{ mA}}.$$

Chapter 4, Solution 1.

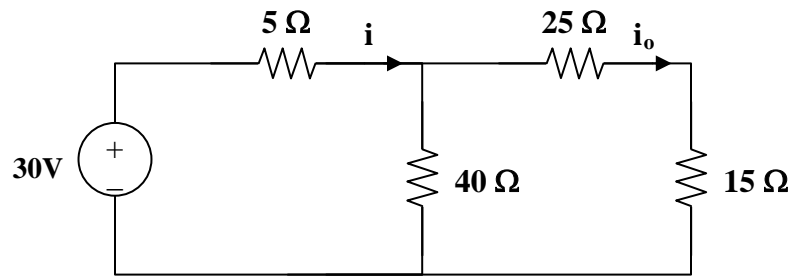

$$40 \parallel (25 + 15) = 20\Omega, \quad i = [30/(5+20)] = 1.2 \text{ and } i_o = i \cdot 20/40 = \mathbf{600 \text{ mA}}.$$

Since the resistance remains the same we get can use linearity to find the new value of the voltage source = $(30/0.6)5 = \mathbf{250 \text{ V}}$.

Chapter 5, Solution 1.

(a) $R_{\text{in}} = \mathbf{1.5\ M\Omega}$

(b) $R_{\text{out}} = \mathbf{60\ \Omega}$

(c) $A = 8 \times 10^4$

Therefore $A_{\text{dB}} = 20 \log 8 \times 10^4 = \mathbf{98.06\ dB}$