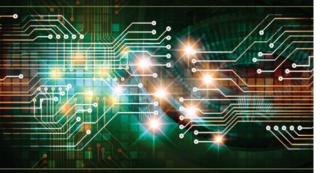


FUNDAMENTALS OF DESIGN AND ANALYSIS



Hernando Lautaro Fernandez-Canque



Analog Electronics Applications

FUNDAMENTALS OF DESIGN AND ANALYSIS



Analog Electronics Applications

FUNDAMENTALS OF DESIGN AND ANALYSIS

Hernando Lautaro Fernandez-Canque

Glasglow Caledonian University, Scotland, United Kingdom



CRC Press Taylor & Francis Group 6000 Broken Sound Parkway NW, Suite 300 Boca Raton. FL 33487-2742

© 2017 by Taylor & Francis Group, LLC CRC Press is an imprint of Taylor & Francis Group, an Informa business

No claim to original U.S. Government works

Printed on acid-free paper Version Date: 20160620

International Standard Book Number-13: 978-1-4987-1495-2 (Hardback)

This book contains information obtained from authentic and highly regarded sources. Reasonable efforts have been made to publish reliable data and information, but the author and publisher cannot assume responsibility for the validity of all materials or the consequences of their use. The authors and publishers have attempted to trace the copyright holders of all material reproduced in this publication and apologize to copyright holders if permission to publish in this form has not been obtained. If any copyright material has not been acknowledged please write and let us know so we may rectify in any future reprint.

Except as permitted under U.S. Copyright Law, no part of this book may be reprinted, reproduced, transmitted, or utilized in any form by any electronic, mechanical, or other means, now known or hereafter invented, including photocopying, microfilming, and recording, or in any information storage or retrieval system, without written permission from the publishers.

For permission to photocopy or use material electronically from this work, please access www.copyright.com/ (CCC), 222 Rosewood Drive, Danvers, MA 01923, 978-750-8400. CCC is a not-for-profit organization that provides licenses and registration for a variety of users. For organizations that have been granted a photocopy license by the CCC, a separate system of payment has been arranged.

Trademark Notice: Product or corporate names may be trademarks or registered trademarks, and are used only for identification and explanation without intent to infringe.

Visit the Taylor & Francis Web site at http://www.taylorandfrancis.com

and the CRC Press Web site at http://www.crcpress.com

To my wife Vicky and our children Lalo, Bruni, Lia, and Mandela



Contents

			xix			
Acknowledg	gments	3	xxi			
Author			xxiii			
Chapter 1	Analog Electronics Applications and Design1					
	1.1	Introd	uction to Analog Electronics1			
	1.2	Analo	g Signals1			
	1.3	Analo	g Systems2			
	1.4	Applic	Application and Design of Analog Systems3			
		1.4.1	Customer Requirements			
		1.4.2	Top-Level Specifications4			
		1.4.3	System Design Approach4			
			1.4.3.1 Top-Level Design5			
			1.4.3.2 Detailed Design5			
		1.4.4	Technology Choice5			
			1.4.4.1 System Testing6			
			1.4.4.2 Social and Environmental Implications6			
			1.4.4.3 Documentation6			
		1.4.5	Distortion and Noise6			
			1.4.5.1 Noise			
			1.4.5.2 Distortion			
		1.4.6	Electronic Design Aids8			
	1.5	Key P	pints9			
Chantan 2	Elas-	hai a Ciana	nite.			
Chapter 2	Electric Circuits					
	2.1 Introduction					
	2.2	Units	11			
		2.2.1	Unit of Charge12			
		2.2.2	Unit of Force12			
		2.2.3	Unit of Energy12			
		2.2.4	Unit of Power			
		2.2.5	Unit of Electric Voltage			
		2.2.6	Unit of Resistance and Conductance			
	2.3	pt of Electric Charge and Current15				
	2.4	Mover	nent of Electrons and Electric Current in a Circuit 16			
		2.4.1	Circuit			
		2.4.2	Electromotive Force			
		2.4.3	Source			
		2.4.4	Load			

viii Contents

	2.5	Passiv	e Compon	ents: Resistance, Inductance, and		
		Capacitance				
		2.5.1	Resistan	ce	17	
			2.5.1.1	Resistors Connected in Series and		
				Parallel	19	
			2.5.1.2	Resistors Connected in Series		
			2.5.1.3	Resistor Connected in Parallel	19	
			2.5.1.4	Special Case		
		2.5.2	Capacita	ance		
			2.5.2.1	Capacitors in Parallel		
			2.5.2.2	Capacitors in Series		
		2.5.3	Inductor	'S		
			2.5.3.1	Inductors in Series	27	
			2.5.3.2	Inductors in Parallel		
			2.5.3.3	Energy Storage W in an Inductor		
		2.5.4	Applicat	tion: Inductive Proximity Sensors		
	2.6		Components of a Circuit: Sources			
		2.6.1		ltage Source		
		2.6.2		l Voltage Source		
		2.6.3		Sources Connected in Series		
		2.6.4		Sources Connected in Parallel		
			2.6.4.1			
			2.6.4.2	Practical Current Source	31	
	2.7	Electr	ic Circuits	/Networks	32	
		2.7.1	Selection	n of Components	34	
	2.8	Key Points				
Chapter 3	Cina	it Analy	rai a		25	
Chapter 3	Circuit Analysis					
	3.1			dy State and Transient Solutions		
	3.2				36	
		3.2.1		ff's Current Law Applied to Electric		
				KCL	36	
		3.2.2		ff's Voltage Law Applied to Electric		
				KVL		
			3.2.2.1	The Voltage and Current Divider		
	3.3	AC Circuits				
		3.3.1		f Phasor Domain		
		3.3.2	1.1	tion of Kirchhoff's Law to ac Circuits		
			3.3.2.1	Impedance Z		
			3.3.2.2	Impedance of an Inductor	65	
			3.3.2.3	Impedance of a Capacitance		
			3.3.2.4	Impedance of a Resistance		
			3.3.2.5	Reactance X		
			3.3.2.6	Polar-Cartesian Forms	69	

Contents ix

			3.3.2.7	Cartesian to Polar Form	69			
			3.3.2.8	Polar to Cartesian	69			
			3.3.2.9	Phasor Diagrams	70			
	3.4	Key Po	oints		76			
Chapter 4	Diodes							
	4.1 Introduction							
	4.2	Semice		Iaterial				
		4.2.1		vity and Energy Bands in Semiconductors				
		4.2.2						
	4.3							
	4.4	Diode	Current-V	oltage Characteristics I–V	81			
		4.4.1		Bias				
		4.4.2	Reverse 1	Bias	82			
	4.5	Differe	ent Types o	f Diodes	83			
		4.5.1		ductor Diodes				
		4.5.2	Zener Di	odes	84			
		4.5.3	Avalanch	e Diodes	84			
		4.5.4	Light-En	nitting Diodes	84			
		4.5.5	Tunnel D	iodes	84			
		4.5.6	Gunn Die	odes	84			
		4.5.7	Peltier D	iodes	84			
		4.5.8	Photodio	des	85			
		4.5.9	Solar Cel	1	85			
		4.5.10	Schottky	Diodes	85			
	4.6	Diode	Applicatio	ns	85			
		4.6.1	Rectifica	tion	85			
		4.6.2	Half-Wav	e Rectifiers	86			
		4.6.3	Full-Wav	e Rectifiers	87			
		4.6.4	Single-Pl	nase Bridge Rectifier Circuit	87			
		4.6.5	Diode as	Voltage Limiter	92			
		4.6.6	Voltage I	Ooubler	93			
	4.7	Testing	g Diodes		94			
	4.8 Key points				94			
	Refe	rence			94			
Chapter 5	Bipol			stor				
	5.1							
	5.2			Transistor				
	5.3			ics				
		5.3.1		r Configurations				
		5.3.2		aracteristics				
		5.3.3	Output C	haracteristics	98			