


M A L V I N O

Electronic PRINCIPLES



SIXTH
EDITION

McGraw-Hill
DONATION

McGraw-Hill
DONATION

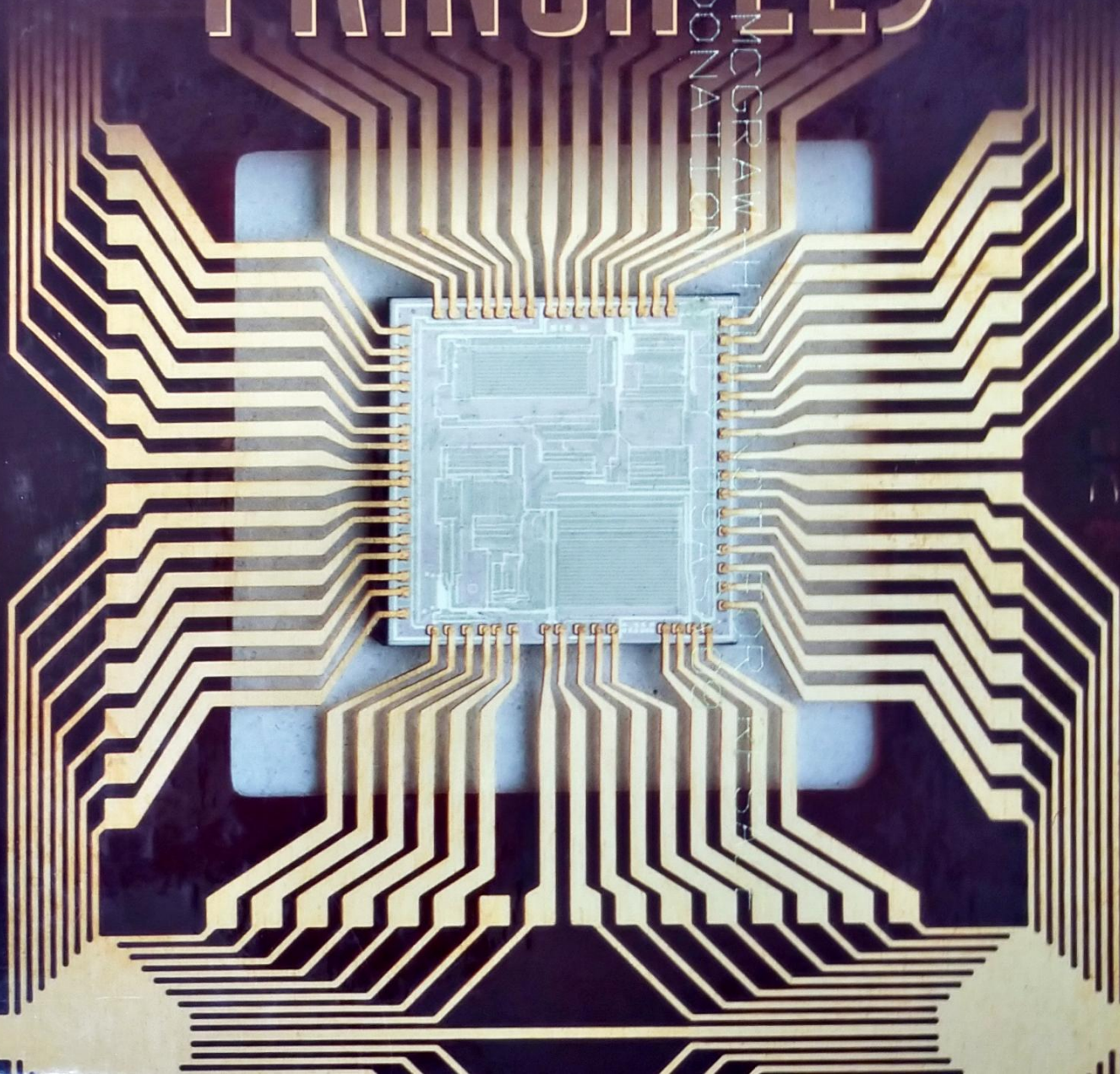

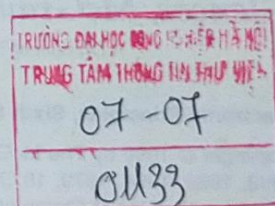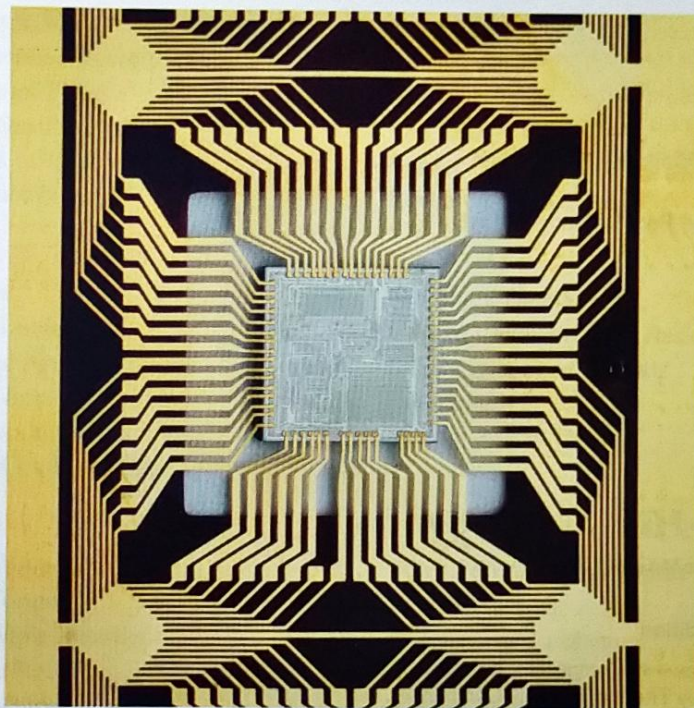M A L V I N O
**Electronic
PRINCIPLES** SIXTH
EDITION



ALBERT PAUL MALVINO, PH.D., E.E.



**Glencoe
McGraw-Hill**



**GIFT OF THE ASIA FOUNDATION
NOT FOR RE-SALE**

**QUÀ TẶNG CỦA QUỸ CHÂU Á
KHÔNG ĐƯỢC BÁN LẠI**

New York, New York Columbus, Ohio Woodland Hills, California Peoria, Illinois

Cover photo: Dick Luria/FPG

Photo credits appear on pages 1011 to 1012, which are hereby made part of this copyright page.

For captions describing the chapter-opening photos, see page 1011.

Library of Congress Cataloging-in-Publication Data

Malvino, Albert Paul.

Electronic principles / Albert Paul Malvino.—6th ed.

p. cm.

Includes index.

ISBN 0-02-802833-3

1. Electronics. I. Title.

TK7816.M25 1999

621.3515—dc21

97-50343

CIP

Glencoe/McGraw-Hill



A Division of The McGraw-Hill Companies

Electronic Principles, Sixth Edition

Copyright © 1999 by The McGraw-Hill Companies, Inc. All rights reserved. Copyright © 1993, 1989, 1984, 1979, 1973 by The McGraw-Hill Companies, Inc. All rights reserved. Printed in the United States of America. Except as permitted under the United States Copyright Act, no part of this publication may be reproduced or distributed in any form or by any means, or stored in a data base or retrieval system, without the prior written permission of the publisher.

Send all inquiries to:
Glencoe/McGraw-Hill
8787 Orion Place
Columbus, Ohio 43240

ISBN 0-02-802833-3 (student edition)

ISBN 0-02-802838-4 (instructor's annotated edition)

890 DOW/DOW 0987654

Contents

ix	Preface	
xii	Chapter 1 INTRODUCTION	
	1-1. The Three Kinds of Formulas	1-5. Thevenin's Theorem
	1-2. Approximations	1-6. Norton's Theorem
	1-3. Voltage Sources	1-7. Troubleshooting
	1-4. Current Sources	
30	Chapter 2 SEMICONDUCTORS	
	2-1. Conductors	2-8. The Unbiased Diode
	2-2. Semiconductors	2-9. Forward Bias
	2-3. Silicon Crystals	2-10. Reverse Bias
	2-4. Intrinsic Semiconductors	2-11. Breakdown
	2-5. Two Types of Flow	2-12. Energy Levels
	2-6. Doping a Semiconductor	2-13. The Energy Hill
	2-7. Two Types of Extrinsic Semiconductors	2-14. Barrier Potential and Temperature
		2-15. Reverse-Biased Diode
62	Chapter 3 DIODE THEORY	
	3-1. Basic Ideas	3-7. Reading a Data Sheet
	3-2. The Ideal Diode	3-8. How to Calculate Bulk Resistance
	3-3. The Second Approximation	3-9. DC Resistance of a Diode
	3-4. The Third Approximation	3-10. Load Lines
	3-5. Troubleshooting	3-11. Surface-Mount Diodes
	3-6. Up-Down Circuit Analysis	
90	Chapter 4 DIODE CIRCUITS	
	4-1. The Half-Wave Rectifier	4-8. Other Power-Supply Topics
	4-2. The Transformer	4-9. Troubleshooting
	4-3. The Full-Wave Rectifier	4-10. Clippers and Limiters
	4-4. The Bridge Rectifier	4-11. Clampers
	4-5. The Choke-Input Filter	4-12. Voltage Multipliers
	4-6. The Capacitor-Input Filter	
	4-7. Peak Inverse Voltage and Surge Current	

144	Chapter 5 SPECIAL-PURPOSE DIODES	
5-1.	The Zener Diode	5-6. Troubleshooting
5-2.	The Loaded Zener Regulator	5-7. Load Lines
5-3.	Second Approximation of a Zener Diode	5-8. Optoelectronic Devices
5-4.	Zener Drop-Out Point	5-9. The Schottky Diode
5-5.	Reading a Data Sheet	5-10. The Varactor
		5-11. Other Diodes
 188	 Chapter 6 BIPOLAR TRANSISTORS	
6-1.	The Unbiased Transistor	6-6. Collector Curves
6-2.	The Biased Transistor	6-7. Transistor Approximations
6-3.	Transistor Currents	6-8. Reading Data Sheets
6-4.	The CE Connection	6-9. Troubleshooting
6-5.	The Base Curve	
 220	 Chapter 7 TRANSISTOR FUNDAMENTALS	
7-1.	Variations in Current Gain	7-7. LED Drivers
7-2.	The Load Line	7-8. The Effect of Small Changes
7-3.	The Operating Point	7-9. Troubleshooting
7-4.	Recognizing Saturation	7-10. More Optoelectronic Devices
7-5.	The Transistor Switch	7-11. Surface-Mount Transistors
7-6.	Emitter Bias	
 258	 Chapter 8 TRANSISTOR BIASING	
8-1.	Voltage-Divider Bias	8-5. Other Types of Bias
8-2.	Accurate VDB Analysis	8-6. Troubleshooting
8-3.	VDB Load Line and Q Point	8-7. PNP Transistors
8-4.	Two-Supply Emitter Bias	
 282	 Chapter 9 AC MODELS	
9-1.	Base-Biased Amplifier	9-6. Two Transistor Models
9-2.	Emitter-Biased Amplifier	9-7. Analyzing an Amplifier
9-3.	Small-Signal Operation	9-8. AC Quantities on the Data Sheet
9-4.	AC Beta	
9-5.	AC Resistance of the Emitter Diode	
 312	 Chapter 10 VOLTAGE AMPLIFIERS	
10-1.	Voltage Gain	10-4. Swamped Amplifier
10-2.	The Loading Effect of Input Impedance	10-5. Two-Stage Feedback
10-3.	Multistage Amplifiers	10-6. Troubleshooting

340	Chapter 11 POWER AMPLIFIERS	
11-1.	Amplifier Terms	11-5. Class C Operation
11-2.	Two Load Lines	11-6. Class C Formulas
11-3.	Class A Operation	11-7. Transistor Power Rating
11-4.	Class B Operation	
378	Chapter 12 EMITTER FOLLOWERS	
12-1.	CC Amplifier	12-6. Biasing Class B Amplifiers
12-2.	Output Impedance	12-7. Class B Driver
12-3.	Maximum Peak-to-Peak Output	12-8. Voltage Regulation
12-4.	Darlington Connections	
12-5.	Class B Push-Pull Emitter Follower	
420	Chapter 13 JFETs	
13-1.	Basic Ideas	13-6. Transconductance
13-2.	Drain Curves	13-7. JFET Amplifiers
13-3.	The Transconductance Curve	13-8. The JFET Analog Switch
13-4.	Biasing in the Ohmic Region	13-9. Other JFET Applications
13-5.	Biasing in the Active Region	13-10. Reading Data Sheets
466	Chapter 14 MOSFETs	
14-1.	The Depletion-Mode MOSFET	14-4. Digital Switching
14-2.	The Enhancement-Mode MOSFET	14-5. CMOS
14-3.	The Ohmic Region	14-6. Power FETs
494	Chapter 15 THYRISTORS	
15-1.	The Four-Layer Diode	15-5. Bidirectional Thyristors
15-2.	The Silicon Controlled Rectifier	15-6. Other Thyristors
15-3.	The SCR Crowbar	15-7. Troubleshooting
15-4.	SCR Phase Control	
524	Chapter 16 FREQUENCY EFFECTS	
16-1.	Frequency Response of an Amplifier	16-7. More Bode Plots
16-2.	Decibel Power Gain	16-8. The Miller Effect
16-3.	Decibel Voltage Gain	16-9. Risettime-Bandwidth Relationship
16-4.	Impedance Matching	16-10. Frequency Analysis of Bipolar Stages
16-5.	Decibels above a Reference	16-11. Frequency Effects of Surface-Mount Circuits
16-6.	Bode Plots	
570	Chapter 17 DIFFERENTIAL AMPLIFIERS	
17-1.	The Differential Amplifier	17-5. Common-Mode Gain
17-2.	DC Analysis of a Diff Amp	17-6. Integrated Circuits
17-3.	AC Analysis of a Diff Amp	17-7. The Current Mirror
17-4.	Input Characteristics of an Op Amp	17-8. The Loaded Diff Amp

616	Chapter 18 OPERATIONAL AMPLIFIERS	
18-1.	Introduction to Op Amps	18-5. Two Op-Amp Applications
18-2.	The 741 Op Amp	18-6. Linear ICs
18-3.	The Inverting Amplifier	18-7. Op Amps as Surface-Mount Devices
18-4.	The Noninverting Amplifier	
662	Chapter 19 NEGATIVE FEEDBACK	
19-1.	Four Types of Negative Feedback	19-5. The VCIS Amplifier
19-2.	VCVS Voltage Gain	19-6. The ICIS Amplifier
19-3.	Other VCVS Equations	19-7. Bandwidth
19-4.	The ICVS Amplifier	
692	Chapter 20 LINEAR OP-AMP CIRCUITS	
20-1.	Inverting-Amplifier Circuits	20-7. Current Boosters
20-2.	Noninverting-Amplifier Circuits	20-8. Voltage-Controlled Current Sources
20-3.	Inverter/Noninverter Circuits	20-9. Automatic Gain Control
20-4.	Differential Amplifiers	20-10. Single-Supply Operation
20-5.	Instrumentation Amplifiers	
20-6.	Summing Amplifier Circuits	
742	Chapter 21 ACTIVE FILTERS	
21-1.	Ideal Responses	21-8. VCVS High-Pass Filters
21-2.	Approximate Responses	21-9. MFB Bandpass Filters
21-3.	Passive Filters	21-10. Bandstop Filters
21-4.	First-Order Stages	21-11. The All-Pass Filter
21-5.	VCVS Unity-Gain Second-Order Low-Pass Filters	21-12. Biquadratic and State-Variable Filters
21-6.	Higher-Order Filters	
21-7.	VCVS Equal-Component Low-Pass Filters	
806	Chapter 22 NONLINEAR OP-AMP CIRCUITS	
22-1.	Comparators with Zero Reference	22-6. Waveform Conversion
22-2.	Comparators with Nonzero References	22-7. Waveform Generation
22-3.	Comparators with Hysteresis	22-8. Another Triangular Generator
22-4.	Window Comparator	22-9. Active Diode Circuits
22-5.	The Integrator	22-10. The Differentiator
854	Chapter 23 OSCILLATORS	
23-1.	Theory of Sinusoidal Oscillation	23-7. The 555 Timer
23-2.	The Wien-Bridge Oscillator	23-8. Astable Operation of the 555 Timer
23-3.	Other RC Oscillators	23-9. 555 Circuits
23-4.	The Colpitts Oscillator	23-10. The Phase-Locked Loop
23-5.	Other LC Oscillators	
23-6.	Quartz Crystals	

906	Chapter 24 REGULATED POWER SUPPLIES	
24-1.	Supply Characteristics	24-5. Current Boosters
24-2.	Shunt Regulators	24-6. DC-to-DC Converters
24-3.	Series Regulators	24-7. Switching Regulators
24-4.	Monolithic Linear Regulators	
956	Appendix A DATA SHEETS	
981	Appendix B MATHEMATICAL DERIVATIONS	
985	Glossary	
997	Answers to Odd-Numbered Problems	
1002	Index	
1011	Captions for Chapter-Opening Photos	
1011	Photo Credits	